
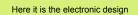


RF field strength meter version 1.

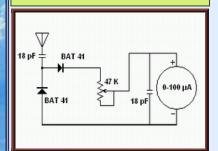I made a RF simple field strength meter for test the remote control from doors ,alarm e.t.c at frequency VHF-UHF, i used one μA meter ,2 diodes ,2 ceramic capacitors,a potentiometer,a box ,and one telescopic antenna. When press the button at remote control,output there is small current RF,where with this simple circuit ,easy i can to know if remote controls it work or no.





Here it is the electronic material, without yet the potentiometer 47 Kohm, 2 capacitor 18 pF,2 diodes BAT 41,and a µA meter



Here it is the plastic box,i have open holes for μA meter ,and i have touch the telescopic antenna



Here with soldering iron the components it is ready



Here it is the sensitivity test





Here it the test with remote temperature /humidity



It is ready



Ready with full open telescopic antenna




Click over to photo for to see a video about it



RF field strength meter version 2.

I made a second version. The electronic design i saw from Here.

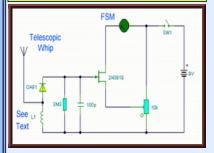Here it is a electronic design.I left the old potentiometer 47 kohm and the μA meter 100 μA .



Here i added a switch on-off,and i put the aerial antenna to other side.



RF field strength meter, It is ready



Here i make a test with mobile phone 1,8 Ghz.

Here i added this electronic material. One transistor JFET 2N3819, one diode germanium AA119, one cap 100 pF, one resistor 3,3 Mohm, one clip 9 volt battery, one battery 9 volt, one switch on-off, and one inductor over ferrite 1,82 μH.



From the other side.



Here i make a test with out remote sensor from weather station at frequency 433 Mhz.



Click here for you see a video

I use a coil over to ferrite about 1,82 μ H (i removed little coil for it is about 1,82 μ H)



I finnish with the soldering iron material.



Here i make a test with remote control 433 Mhz





